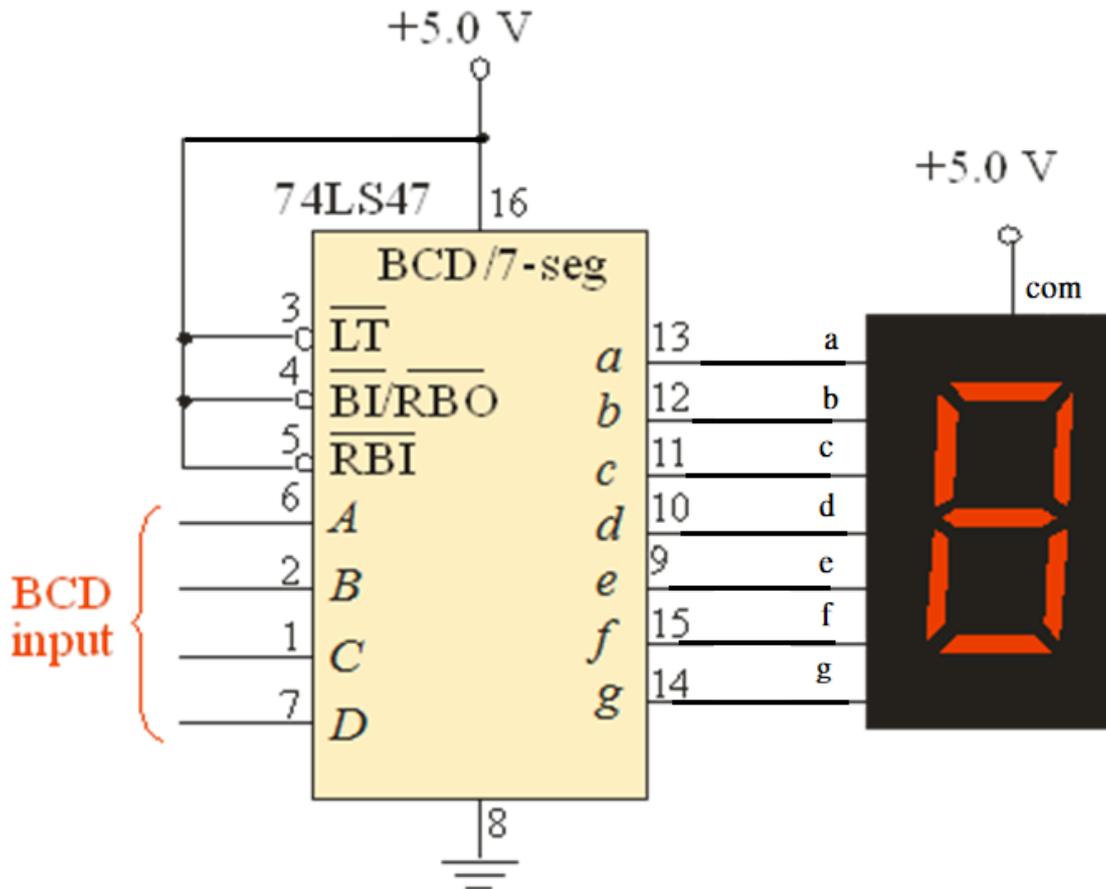
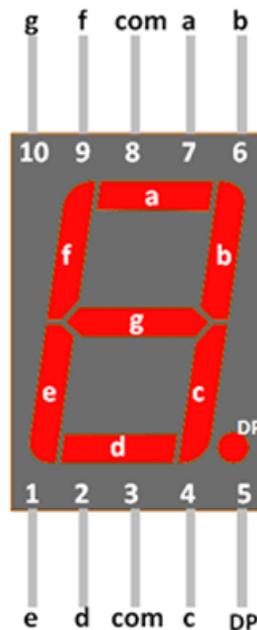


Interfacing IC7447 with Seven Segment Display (Common Anode)



Note: In the above diagram, BCD input D is the least significant bit (LSB), and A is the most significant bit (MSB)

Pin details of Seven Segment Display (Common Anode)



Note: Use the dot marking as a reference to identify the correct pin orientation of the display.